

AC signals

So far we have studied operaⁿ of circuit with DC signal, now we will provide ^{for} sinusoidal signal as input.

$$V(t) = V_m \sin(\omega t)$$


↳ nature

V_m = Amplitude

ω = frequency

t = time

ωt = argument

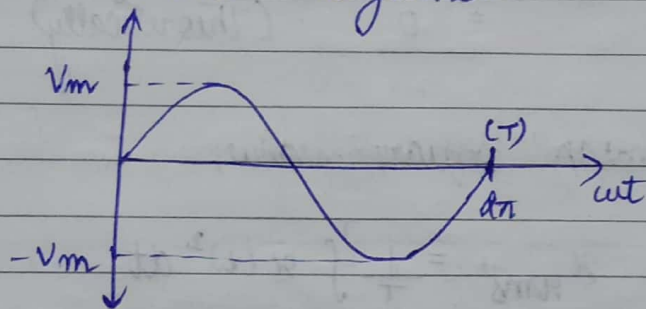

$$\omega T = 2\pi$$

$$\omega = \frac{2\pi}{T}$$

$$\omega = 2\pi f$$

$$2\pi \text{ (rad)} = 360^\circ$$

$$1 \text{ rad} = 57.3^\circ$$

conversion factor

$\text{rad} = \frac{\pi}{180} \times ^\circ$ $^\circ = \frac{180}{\pi} \times \text{rad}$

✓ Average value of Alternating signal:

In general, average value of general signal $x(t) = \frac{1}{T} \int_0^T x(t) dt$

$$V_{avg} = \frac{1}{\pi} \int_0^{\pi} V_m \sin d(\omega t) \\ = 0.63 V_m$$

$$\text{for } V_{avg} = \frac{1}{\pi} \int_0^{2\pi} V_m \sin d(\omega t) \\ = 0 \quad (\text{Theoretically})$$


Root mean square value,

$$x_{rms} = \frac{1}{T} \int_0^T x(t)^2 dt$$

$$V_{rms} = \frac{1}{2\pi} \int_0^{2\pi} (V_m \sin \omega t)^2 d(\omega t) \\ = 0.707 V_m$$

✓ response of AC signal in inductor or capacitor:

i)

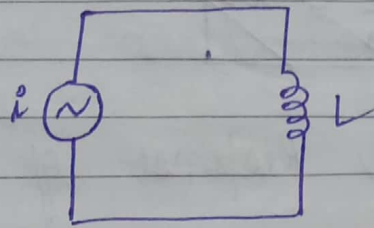

(lags by 90°)

$$i = I_m \sin \omega t$$

$$V = L \frac{di}{dt}$$


$$V = \omega L I_m \cos \omega t$$

$$= V_m \sin (\omega t + 90^\circ)$$

$$V_m = \omega L I_m$$

$$\boxed{\frac{V_m}{I_m} = \omega L}$$

ii)

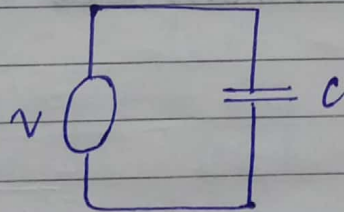

(leads by 90°)

$$V = V_m \sin \omega t$$

$$i = C \frac{dV}{dt}$$

$$i = \omega C V_m \cos \omega t$$

$$i = I_m \cos \omega t$$

$$i = I_m \sin (\omega t + 90^\circ)$$


$$I_m = \omega C V_m$$

$$\boxed{\frac{I_m}{\omega C} = \frac{V_m}{I_m}}$$

$$V_m = \omega L I_m$$

$$\frac{V_m}{I_m} = \omega L$$

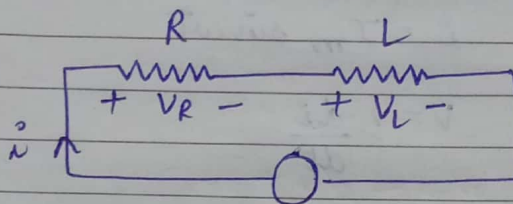✓ # Sinusoidal Response of series R-L circuit:



$$V_R = iR = R I_m \sin \omega t$$

$$V_L = \omega L I_m \sin(\omega t + 90^\circ)$$

$$V = V_R + V_L$$

$$V_m \sin(\omega t + \theta) = R I_m \sin(\omega t) + \omega L I_m \sin(\omega t + 90^\circ)$$

↑
phase shift

$$V_m \sin \omega t \cos \theta + V_m \sin \theta \cos \omega t = R I_m \sin \omega t + \omega L I_m \sin \omega t \cos 90^\circ + \omega L I_m \sin 90^\circ \cos \omega t$$

here,

$$V_m \cos \theta = R I_m$$

$$V_m \sin \theta = \omega L I_m$$

$$V_m^2 = (R I_m)^2 + (\omega L I_m)^2$$

$$V_m = I_m \sqrt{R^2 + (\omega L)^2}$$

$$V_m = I_m \underbrace{\sqrt{R^2 + (\omega L)^2}}_{\text{impedance}}$$

lag by $\frac{\omega L}{R}$

→

$$R + j\omega L$$


$$\sqrt{R^2 + (\omega L)^2} \angle \tan^{-1}\left(\frac{\omega L}{R}\right)$$

$$Z = \sqrt{R^2 + (\omega L)^2} \angle \tan^{-1}\left(\frac{\omega L}{R}\right)$$

$$I_m = \frac{V_m}{Z} = \frac{V_m}{\sqrt{R^2 + (\omega L)^2}} \angle -\tan^{-1}\left(\frac{\omega L}{R}\right)$$

✓ #

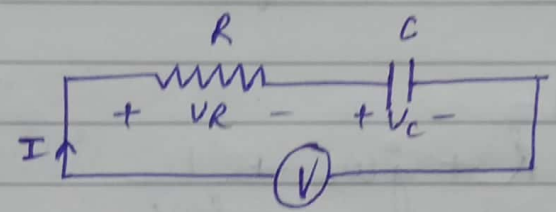Sinusoidal Response of series R-C circuit:



$$V = V_m \sin \omega t$$

$$V = I \left(R + \frac{1}{j\omega C} \right)$$

$$V = I \left[R - \frac{j}{\omega C} \right]$$

$$Z = R - \frac{j}{\omega C}$$

$$Z = \sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2} \angle -\tan^{-1} \frac{1}{\omega R C}$$

current leads by $\frac{1}{\omega R C}$


$$I = \frac{V}{Z}$$

$$= \frac{V}{\sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2} \angle -\tan^{-1} \frac{1}{\omega R C}}$$

$$= \frac{V}{\sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}} \angle \tan^{-1} \left(\frac{1}{\omega R C} \right)$$

$$\begin{aligned} X_C &= \frac{1}{\omega C} \\ &= \frac{1}{0} \\ &= \infty \end{aligned}$$

✓ + Series RLC circuit :

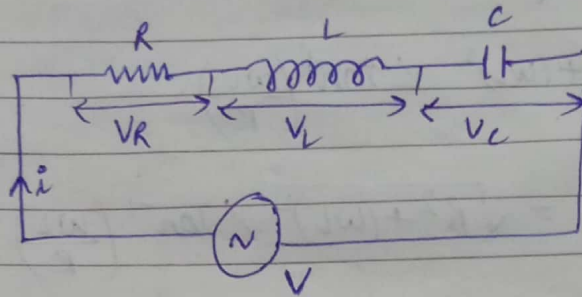

$$V = V_R + V_L + V_C$$

$$= iR + iX_L + iX_C$$

$$= i \left(R + j\omega L + \frac{1}{j\omega C} \right)$$

$$\begin{cases} X_L = j\omega L = jX_L \\ X_C = \frac{1}{j\omega C} \approx \frac{-j}{\omega C} = -jX_C \end{cases}$$

$$V = IZ$$

$$Z = R + j\omega L + \frac{1}{j\omega C}$$

$$Z = R + j\omega L - \frac{j}{\omega C}$$


$$Z = R + j \left(\omega L - \frac{1}{\omega C} \right)$$

$$\text{mag.} = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C} \right)^2}$$


$$\tan^{-1} \left(\frac{\omega L - \frac{1}{\omega C}}{R} \right)$$

① circuit becomes inductive when $\omega L > \frac{1}{\omega C}$

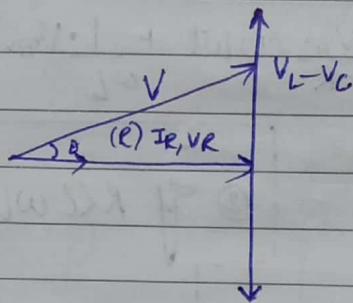② circuit becomes capacitive $\frac{1}{\omega C} > \omega L$




(Inductive)

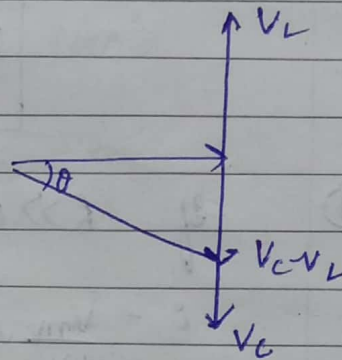

(capacitive)

* Sinusoidal response of R-L ckt

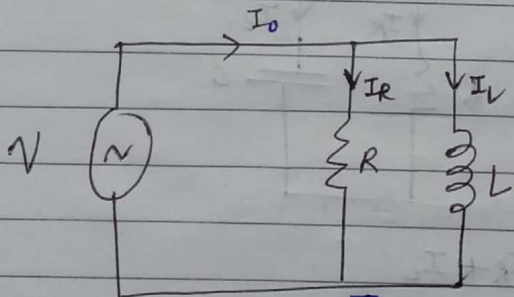

$$V = V_m \sin \omega t$$

$$I_0 = I_L + I_R$$

$$I_R = \frac{V_m \sin \omega t}{R} = \frac{V}{R} \quad \left| \quad I_L = \frac{V}{X_L} \right|$$

$$I_0 = \frac{V}{R} + \frac{V}{X_L} = I$$

$$I_0 = V \left(\frac{1}{R} + \frac{1}{j\omega L} \right)$$

opposite of
impedance

admittance $\rightarrow$

$$\left(I = \frac{V}{Y} \right)$$

$$Y = \frac{1}{R} + \frac{1}{j\omega L} = \frac{1}{R} - \frac{j}{\omega L}$$

Sinusoidal i/p, $v = v_m \cos \omega t$

$$I = I_R + I_L$$

$$I = \frac{v}{R} + \frac{1}{L} \int v dt$$

$$I = \frac{V_m \cos \omega t}{R} + \frac{1}{\omega L} V_m \sin \omega t$$

① if $R \gg \omega L$


② if $R \ll \omega L$

Phase

$$i = \frac{V_m \cos (\omega t - 90^\circ)}{\omega L}$$

$$i = \frac{V_m \cos \omega t}{R}$$

Sinusoidal series of RLC circuit.

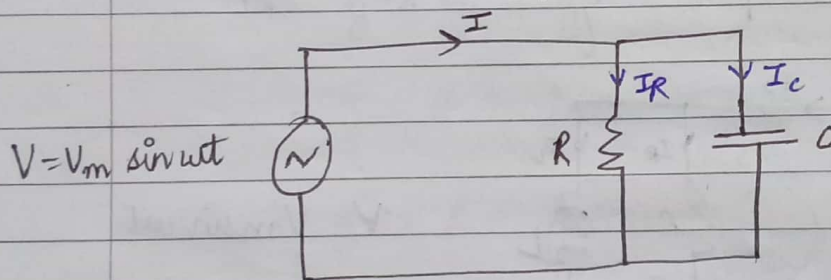

$$I = I_R + I_C$$

$$I = \frac{v}{R} + \frac{1}{\omega C} \frac{dv}{dt}$$

$$I = \frac{v}{R} + jv\omega C$$

$$I = I_R + I_C$$

$$= \frac{V_m \sin \omega t}{R} + C \frac{dv}{dt}$$

$$= \frac{V_m \sin \omega t}{R} + \omega C V_m \cos \omega t$$


i) if $R \gg X_C$

$$i = i_C = \omega C V_m \sin(\omega t + 90^\circ)$$

ii) if $R \ll X_C$

$$i \approx i_R \approx \frac{V_m}{R} \sin \omega t$$

Sinusoidal series of RLC circuit

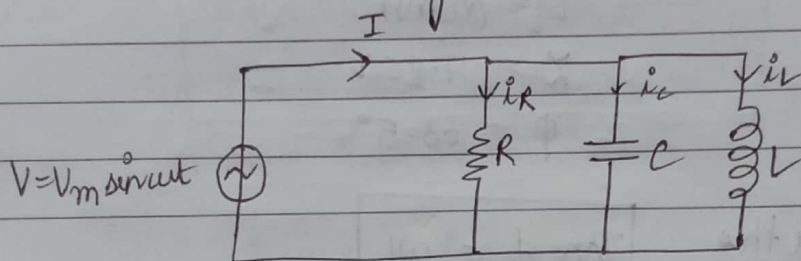

$$I = i_R + i_C + i_L$$

$$I = \frac{V}{R} + \frac{V}{X_C} + \frac{V}{X_L}$$


$$I = \frac{V_m \sin \omega t}{R}$$

$$I = \frac{V}{R} + \frac{V}{j\omega L} + \frac{V}{\frac{1}{j\omega C}}$$

$$I = \frac{V}{R} + \frac{V}{j\omega L} + Vj\omega C$$

$$I = \frac{V}{R} + \frac{1}{L} \int V dt + C \frac{dV}{dt}$$
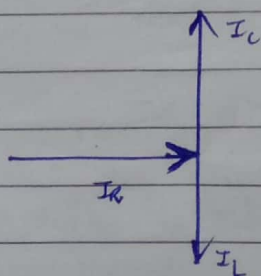
$$= \frac{V_m \sin \omega t}{R} - \frac{V_m \cos \omega t}{\omega L} + V_m \omega C \cos \omega t$$



(all values in rms)

Q In a R-L circuit the inductance being 20 millihenry (mH), impedance 17.85Ω & angle of the lag of the input current from the applied voltage. find the value of R & L .

$$\omega = 796.875 \text{ rad/s}$$

$$R = 8 \Omega$$

$$L = 20 \text{ mH}$$

$$Z = 17.85 \Omega$$

$$\phi = 63.5^\circ$$

Use this

$$\tan \phi = \frac{\omega L}{R}$$

Q Applied voltage is 11^t RLC circuit is given by,

$$v = 50 \sin (5000t + \frac{\pi}{4}) \text{ V}$$

$$R = 20 \Omega$$


$$L = 1.6 \times 10^{-3} \text{ H}$$

$$C = 20 \mu \text{ F}$$

find total current?

$$I = 1.975 \angle 18.5^\circ \text{ A}$$

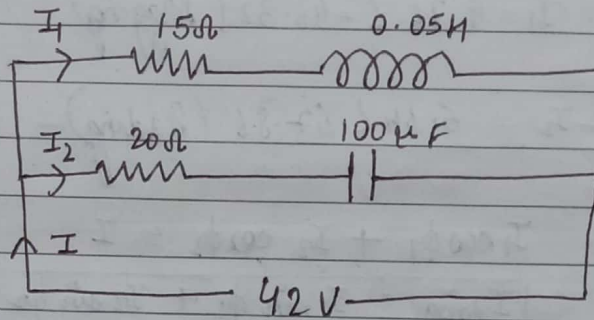Q Determine rms value of current in each branch and total current of the circuit draw its phasor diagram.



$$f = 50 \text{ Hz}$$

$$Z_1 = R_1 + j\omega L_1$$

$$= 15 + j(2\pi) \times 50 \times 0.05$$

$$= 15 + j(15.71)$$

$$Z_1 = \sqrt{(15)^2 + (15.71)^2}$$

$$= 21.72 \Omega$$

$$\tan^{-1} \left(\frac{15.71}{15} \right) = \angle 46.32^\circ \text{ (lagging voltage)}$$

$$Z_2 = 20 + (-j) \frac{1 \times 10^4}{2\pi \times 50 \times 100 \times 10^{-6}}$$

$$= 20 + (-j) \times \frac{100}{\pi}$$

$$= 20 - 31.81j$$

$$|Z_2| = 37.58$$

$$\angle 57.86^\circ \text{ (leading)}$$

$$I_1 = \frac{V}{Z_1} = \frac{212}{21.72 \angle 46.32}$$

$$I_2 = \frac{212}{37.58}$$

$$\angle 57.86$$

$$I_1 = 9.76 \angle -46.32 \text{ (lagging)}$$

$$I_2 = 5.64 \angle 57.86 \text{ (leading)}$$

$$I_1 \cos \phi_1 + I_2 \cos \phi_2 = I$$

$$I_{\text{img}} = I_1 \sin \phi_1 + I_2 \sin \phi_2$$

$$I = I_R + j I_{\text{img}}$$


$$\phi = \tan^{-1} \left(\frac{I_I}{I_R} \right)$$

$$I_{\text{Real}} = 9.76 \cos(46.32) + 5.64 \cos(57.86) \\ = 9.74$$

$$I_{\text{img}} = -2.28$$


$$\phi = \tan^{-1} \left(\frac{I_{\text{img}}}{I_R} \right) = -13.17^\circ$$

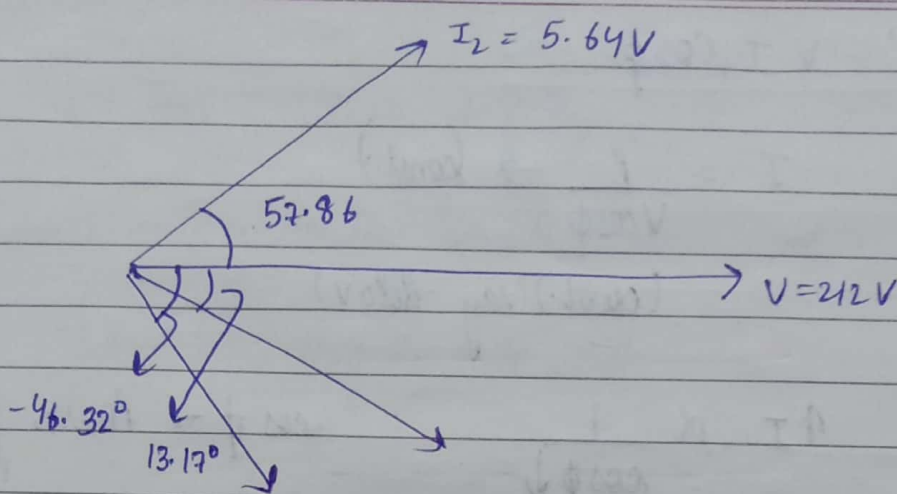Reference line (which is common) in this case voltage is common.



$$\frac{1}{X_L} = \text{susceptance}$$

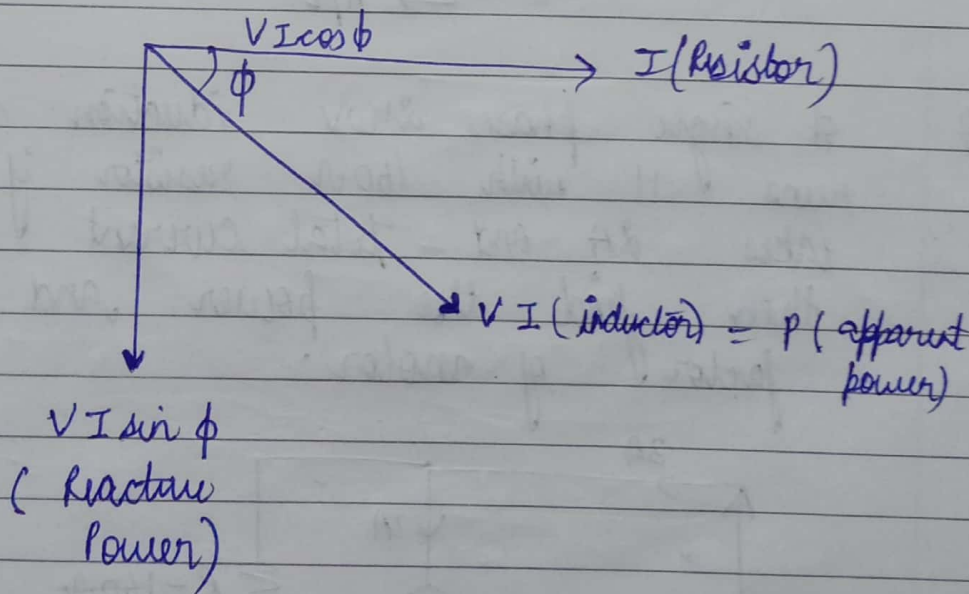✓ Conductance + susceptance = admittance (Z^{-1})
 (X_C & X_L)⁻¹
 Real / actual / active power



Resistor also has $P = VI \cos \phi$
 But ϕ is 0

Real power $\rightarrow$ power consumed by load
 Reactive power $\rightarrow$ not consumed by load.

$$P = V I \cos \phi$$

$$I = \frac{P}{V \cos \phi} \rightarrow (\text{const.})$$

(const.) (say 240V)


$$\uparrow I \propto \frac{1}{\cos \phi \downarrow} \quad \cos \phi \rightarrow \text{Power factor}$$

If $\cos \phi < 1$, i increases (i.e. equip is drawing more current from source)

Real power consumed by inductor / capacitor = 0

$$\frac{V I \cos \phi}{\rightarrow \pi/2}$$

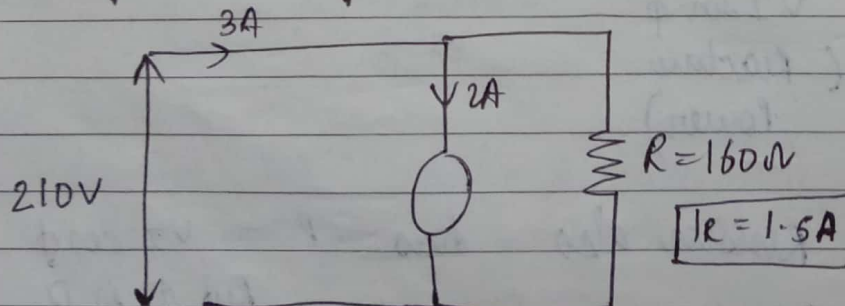Q A single phase 240V induction motor runs in parallel with 160Ω resistor if motor takes 2A and total current is 3A, then find the power and power factor of motor.




there will be lagging power factor in motor since more current is drawn than should be

$$I_m = I_{wt} + j I_r$$

$$I_m + I_r = 3A$$

$$I_w + j I_u + I_r = 3$$

Series Resonance:

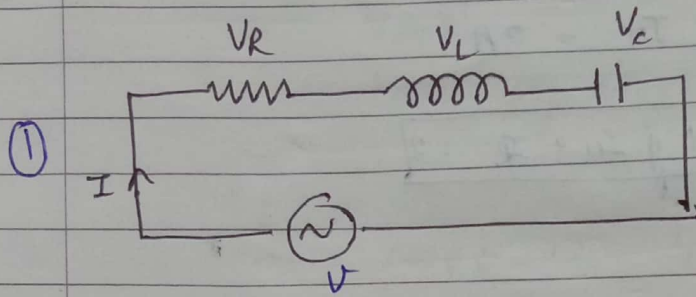

$$I = \frac{V}{Z}$$

$$Z = R + j\omega L + \frac{1}{j\omega C}$$

$$Z = R + j(X_L - X_C)$$

$$I = \frac{V}{R + j(X_L - X_C)}$$

at resonance

$$X_L = X_C$$

$$I = \frac{V}{R}$$

② $\cos \phi = \frac{R}{Z}$

$$X_L = X_C$$


$$\omega L = \frac{1}{\omega C}$$

$$\omega^2 = \frac{1}{LC}$$

$$\omega = \frac{1}{\sqrt{LC}}$$

③

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

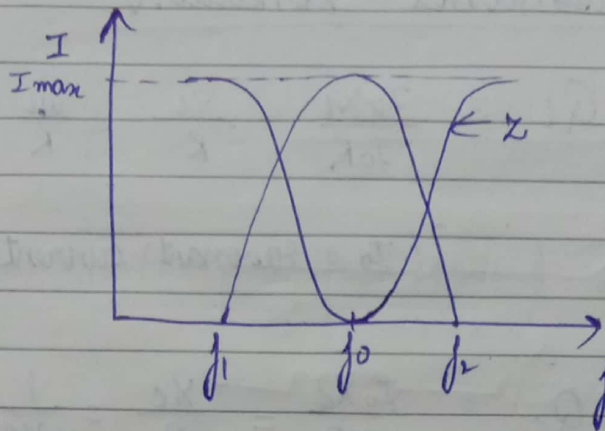

f_1 & f_2 : half power frequency
 lower half power $\vee$ higher half power $\vee$

Q factor at resonance:

$$Q = \frac{V_L}{V} = \frac{V_C}{V}$$

When not
in resonance
condition

$$Q_L = \frac{I_L \times R}{I \times R} = \frac{I_L \times X_L}{I \times R} = \frac{I_L \times X_L}{I R}$$

$$Q_C = \frac{I_C \times X_C}{I \times R} = \frac{I_C \times X_C}{I R}$$

$$Q = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 R C}$$

In resonance condition:

$$Q_L = \frac{I_0 X_L}{I_0 R} = \frac{X_L}{R} = \frac{\omega L}{R} = \frac{1}{\sqrt{LC}} \cdot \frac{L}{R} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

(I_0 = resonant current)

$$Q_C = \frac{I_0 X_C}{I_0 R} = \frac{X_C}{R} = \frac{1}{\omega_0 R C} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

(I_0 = resonant current)

✓ Bandwidth of series resonating ckt →

at resonance : $X_L = X_C$

at half power :

$$X = \pm (X_L - X_C) = R$$

higher ω X_L exceed X_C

lower " X_C " X_L

for f_2 $\left(\omega_2 L - \frac{1}{\omega_2 C} \right) = R$ — (1)

for f_1 $\left(\omega_1 L - \frac{1}{\omega_1 C} \right) = -R$ — (2)

(Book में काफी दूरे पर जितना class में
करवाया है उतना ही करना)

Page No. _____

Date _____

Adding ① & ②,

$$(\omega_2 + \omega_1)L - \frac{1}{C} \left(\frac{\omega_1 + \omega_2}{\omega_1 \omega_2} \right) = 0$$

$$L = \frac{1}{C} \left(\frac{1}{\omega_1 \omega_2} \right)$$

$$\boxed{\omega_1 \omega_2 = \frac{1}{LC}} \quad \text{--- ③}$$

Subtracting ① & ② and divide by L:

then we'll get

$$\boxed{(\omega_2 - \omega_1) = \frac{R}{L}} \quad \text{--- ④}$$

$$Q = \frac{\omega_0 L}{R}$$

$$\boxed{\frac{R}{L} = \frac{\omega_0}{Q}} \quad \text{--- ⑤}$$

from eqⁿ --- ④



$$\omega_2 - \omega_1 = \frac{\omega_0}{Q}$$

$$\boxed{Q = \frac{\omega_0}{\omega_2 - \omega_1}} \quad \boxed{= \frac{f_0}{f_2 - f_1}} \quad \boxed{= \frac{\text{resonant } \omega}{\text{Bandwidth}}}$$

Imp. 0 Derivation of calculating Bandwidth

Date

Parallel resonance

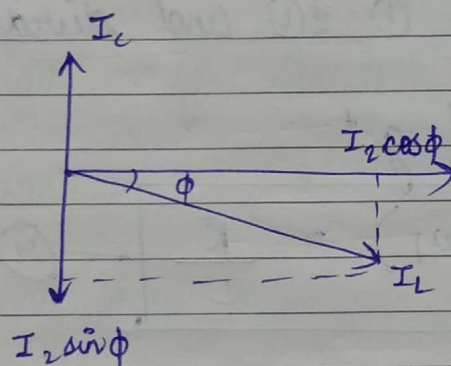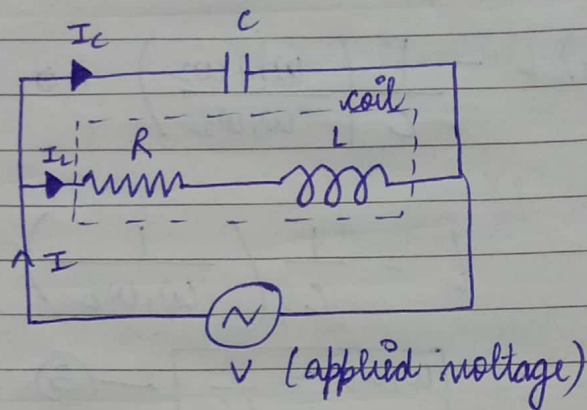

$$I = I_L \cos \phi$$

★ Resonance, तब आवृत्ति जब imaginary part zero होता


∴ at resonance,

$$I_C = I_L \sin \phi$$

$$\frac{V}{X_C} = \frac{V}{(R + jX_L)} \times \frac{X_L}{Z_L}$$

$$R + jX_L = Z_L$$

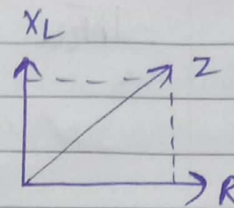
$$\frac{V}{X_C} = \frac{V}{Z_L} \times \frac{X_L}{Z_L}$$




$$f_0 = \frac{1}{2\pi L} \sqrt{\frac{L}{C} - R^2}$$

$$\frac{V}{Z_{in}} = \frac{V}{Z_L} \times \frac{R}{Z_L}$$


$$Z_{in} = \frac{L}{C R}$$

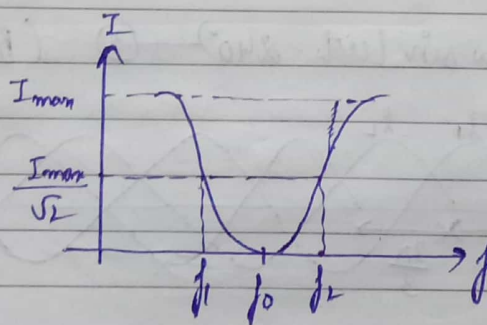

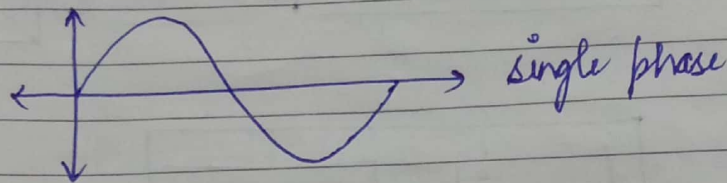Three phase signals (for uninterrupted power supply)



→ generation:


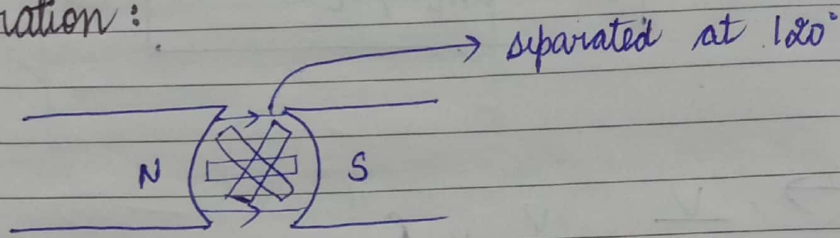



$$e = - \frac{d\phi}{dt}$$

$$e_1 = E_m \sin \omega t \text{ --- ① (Red colour)}$$


$$e_2 = E_m \sin(\omega t - 120^\circ) \text{ --- ② (Yellow colour)}$$
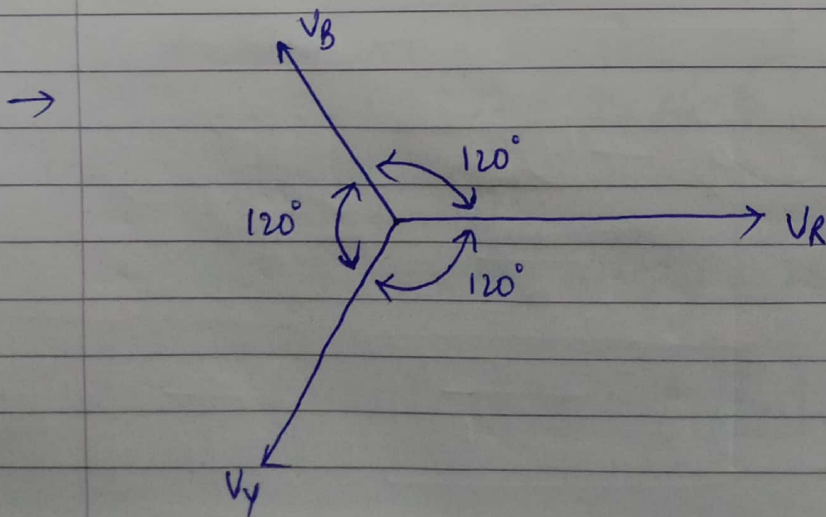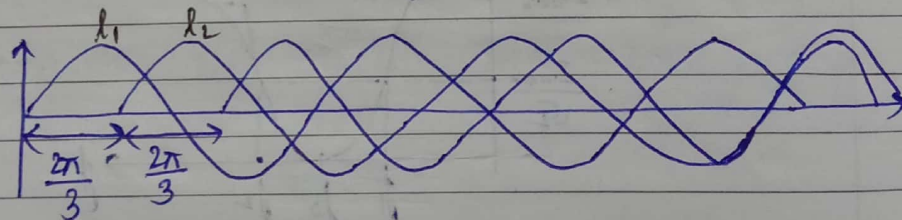
$$e_3 = E_m \sin(\omega t - 240^\circ) \text{ --- ③ (Blue colour)}$$



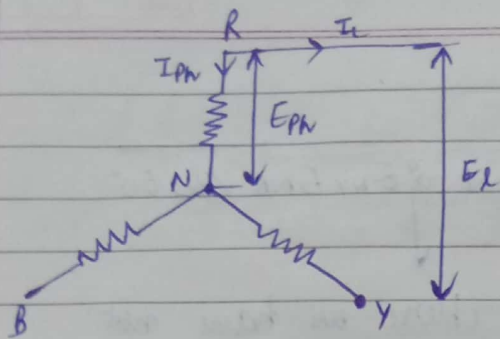

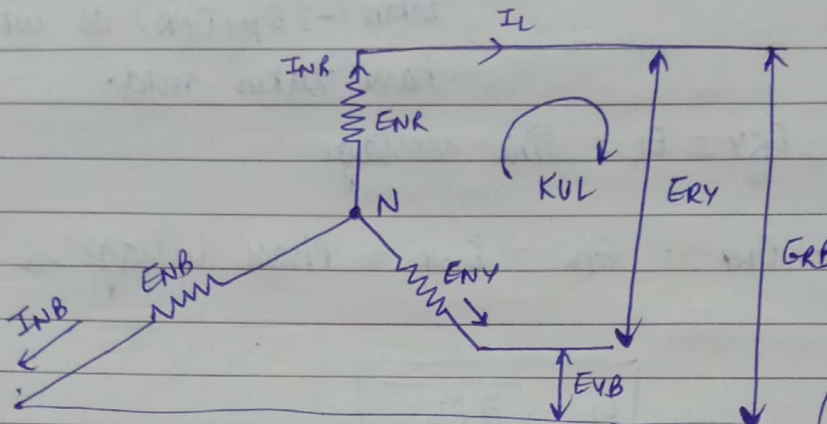$I_L = \text{line current} = I_{NR}$
 $\Rightarrow \text{Phase current}$




(all parts are identical)

$$\vec{E}_{NR} + \vec{E}_{RY} - \vec{E}_{NY} = 0$$

$$\vec{E}_{NR} + \vec{E}_{RY} = \vec{E}_{NY}$$
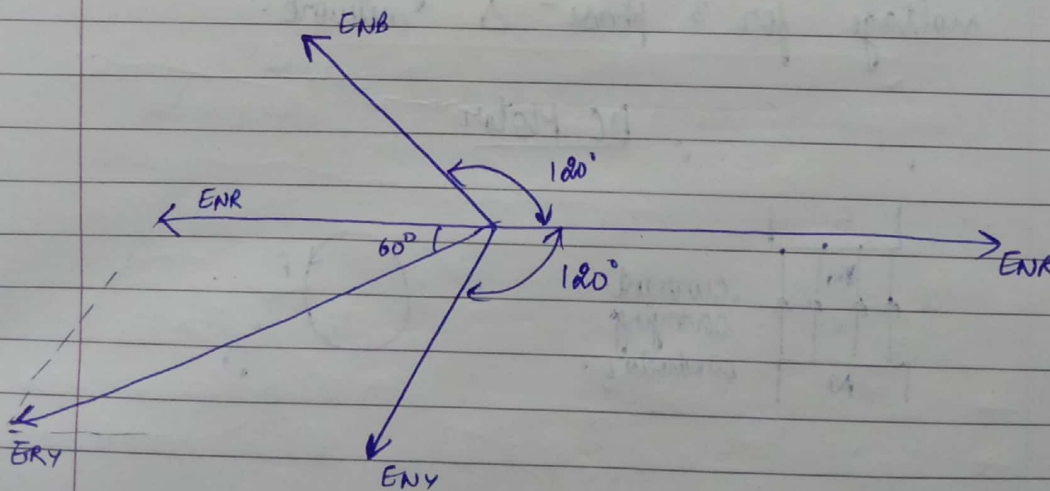
$$\vec{E}_{RY} = \vec{E}_{NY} - \vec{E}_{NR}$$



By Ilgm law:

$$E_{RY} = \sqrt{E_{NY}^2 + E_{NR}^2 + 2E_{NY}E_{NR}\cos 60^\circ}$$

(Here we have not taken $-2E_{NY}E_{NR}$ as we have taken med.)

$$E_{RY} = E_L = \text{line voltage}$$



if given points are identical $\leftarrow E_{NY} = E_{Ph} = E_{NR} = \text{Phase voltage}$


$$E_L = \sqrt{3} E_{Ph}$$

$$E_L = \sqrt{3} E_{Ph}$$

Q find relationship ① line current and phase current, ② line voltage and phase voltage for 3 phase Δ network.

DC Motor

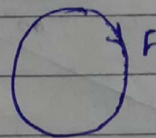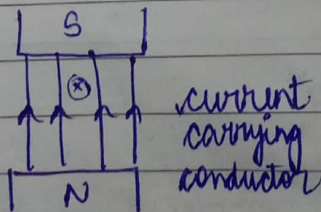

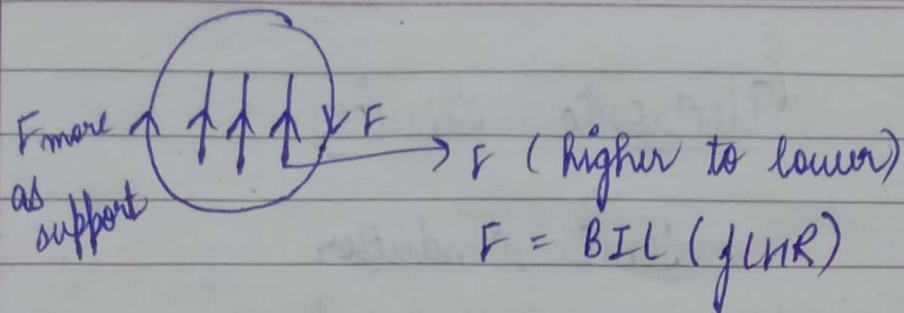

Back emf


$$E_b = \frac{\phi P N Z}{60 A}$$

ϕ = flux

P = no. of poles

N = speed of rotation of conductor

A = no. of parallel paths

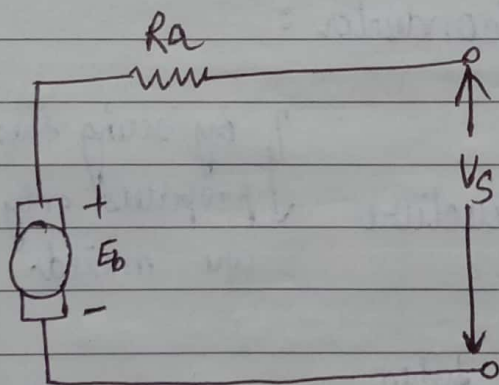

(I_a = armature current)

$$V_s = E_b + I_a R_a + V_{brush}$$